NYCU RF Design Mid-Term Exam

2023/05/01

(10%) In ETSI about receiver characteristics the requirements are given in terms of
power levels at the antenna connector of the receiver. Equipment with integral antenna
may be taken into account by converting these power level requirements into field
strength requirements, assuming a 0 dBi gain antenna. Please verify the fields strengths
E(dBuV/m) related to the power levels P (dBm) under 50 ohms impedance by the
following formula


E (dBuV/m) = P(dBm) + 20logF(MHz) + 77.2


Where F is the operating frequency in MHz.

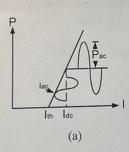2. (10%) The typical characteristic of output light power P vs. input current I of laser diodes under forward bias is shown in the following figure (a) where I_{th} is the threshold current. This diode can be amplitude-modulated directly from a RF signal source through a bias-T network as shown in figure (b). The Modulation Index m is defined as


$$m = \frac{I_{ac}}{I_{dc} - I_{th}}$$

Where I_{ac} is the ac current, I_{dc} is the DC bias current. Assume the dynamic resistance equal to 5Ω with I_{th} =20mA and I_{dc} =50mA, find the setting of the RF output power at the front panel to obtain m=80%.




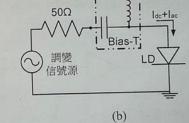

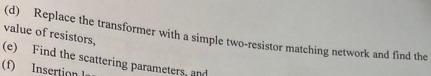
- 3. (30%) A load R_L =200 Ω is wanted to match the rf source with Rs=50 Ω internal impedance. Two methods of wide-band matching are considered. One is to use the transformer, which is lossless and is generally used as a calibrator for insertion loss measurement. The other is to use a resistive network, however with certain loss. Please answer the following questions:
 - (a) Find the turn ratio of transformer primary to secondary=1:n for power matching,
 - (b) Find the scattering parameters for the transformer with characteristic impedances at input port and output port equal to Rs and R_L, respectively,
 - (c) Verify the insertion loss equal to 0dB



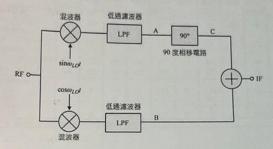- (e)
- Find the scattering parameters, and Insertion loss. (f)
- 4. (10%) The block diagram in the following is the well-known Hartley image rejection mixer. The RF input contains both desired signal and image noise. $RF\ Signal = A_{RF}\cos(\omega_{RF}t) + A_{im}\cos(\omega_{im}t)\ .\ \ Assume\ \ \omega_{RF} < \omega_{LO} < \omega_{im}\ .$
 - (a) Can you obtain the desired signal at IF port? (b) If not, how to modify the block



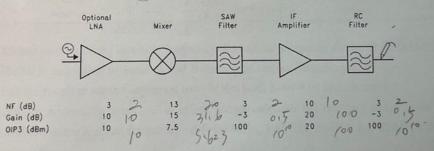5. (20%) The rf link budget is shown in the figure. The noise figure, gain, and OIP3 in each block are also indicated. Assume input power equal to -93dBm, Find (a) input-referred total NF, (b) total gain, (c) total output power, and (d) total output OIP3.



- 6. (20%) The frequency bands (I), receiver blocking levels (II), and transmitter spurious (III) for DCS-1800 are listed as follows.
 - (I) Frequency Band:
 - 1710 MHz to 1785 MHz: Up Link;
 - 1805 MHz to 1880 MHz: Down Link.
 - (II) Blocking characteristics

The blocking characteristics of the receiver are specified separately for in-band and outof-band performance as identified in the following table-A and table-B.

Table-A Frequency Band for blocking sig

Frequency	Frequency r	ange (MHz)	
band	DCS	800	
in-band out-of-band (a) out-of-band (b) out-of band (c) out-of band (d)	1 785 - 1 920 0,1 - 1705 > 1 705 - < 1 785 > 1 920 - 1 980 > 1 980 - 12,750	BTS 1 690 - 1 805 0.1 - < 1 690 N/A N/A > 1 805 - 12,750	

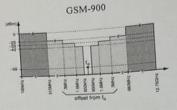


Table-B Blocking Level

Frequency	GSM 400, P-, E- and R-GSM 900					0	DCS 1 800 & PCS 1 900				
band	other MS small MS		IMS	BTS		MS		BTS			
	dBµV (emf)		dBµV (emf)	dBm	dBµV (emf)	dBm	dBµV (emf)	dBm	dBµV (emf)	dBm	
in-band		The same		122	2200	1	70	- 10	78	-35	
600 kHz ≤ f-f ₀ <	75	-38	70	-43	87	-26	70	-43	10	*35	
800 kHz 800 kHz ≤ f-f ₀ <	80	-33	70	-43	97	-16	70	-43	88	-25	
1,6 MHz		-			1			1		1	
1,6 MHz ≤ f-f0 < 3 MHz	90	-23	80	-33	97	-16	80	-33	88	-25	
3 MHz ≤ f-f0	90	-23	90	-23	100	-13	87	-28	88	-25	
out-of-band	24523	100		0	121		113	0	113	10	
(a)	113	0	113	1 0	121	8	101	00 2532	10000000	1 .	
(b)		-	1				101			1 .	
(c)	100		1	0	121	8	113				
(d) NOTE: For definition of	113	0	113			0	1114	-			


(III) Transmitter Spurious Emission Measurement 4.3.3.1

Table-C

Band	Frequency offset	Measurement bandwidth		
Ballu	(offset from carrier)	30 kHz		
relevant transmit	≥ 1,8 MHz	***************************************		
band	≥ 6 MHz	100 kHz		


- Please plot blocking levels in frequency domain as reference shown from 0.1MHz to 12.750MHz according to Table-A and B for MS at carrier frequency f_{o} .
- (b) Let the receiver sensitivity equal to -99dBm with S/N=9dB and channel BW=200kHz. According to reciprocal effect, please calculate the required phase noise of local oscillator at each offset frequency Δ f=0.6MHz, 1.6MHz, 3MHz, and 20MHz, due to blocking effect.
- (c) The local oscillator is also used in the transmitter mode. The phase noise is therefore limited by the spurious emission, especially near the band edge. In DCS-1800 the spurious level should be less than -71dBm in the receiver band 1805-1880MHz [3GPP TS-0505 4.3.3.1]. The measurement bandwidth depends on the offset frequency as listed in the Table-C. Please calculate the required phase noise for the transmitter mode at edge 1785MHz with output power +33dBm.
- (d) Furthermore, compare and indicate which one between questions (b) and (c) is the most stringent in phase noise under the Leeson model with offset (Δf)⁻² shaping.

由公式 学位输入功率= 上 = 上 Cr= Ex SA $= \frac{g \lambda^2 E^2}{480 \Pi^2} = \frac{g C^2 E^2}{480 \Pi^2 E^2}$ 1 9=1= 0 dBi $\frac{C^2 E^2}{480 \pi^2 F^2} \times 1000 \, (mW)$ $= \frac{(3\times10^8)^2}{480\pi^2} \frac{E^2(4\%)\times10^{12}}{F^2_{\text{mHz}}\times10^{12}} \times 10^{12}$ = 1.9×108 = (NV/m) F2 (MHz) 取由 E (dB w/m) = Pr (dBm)+20log F(MHz)+77.2 别試天線的設備心災考處天線場強度, 频率越大,则天線場強度越大 2. 由公式和 Iac=a8x (Ide-Ich) = 24mA J. VS, P= 1.32V Vrms = 1.32 JBm=10/g (1/2/2) 10.00]=6.39 (JBm)

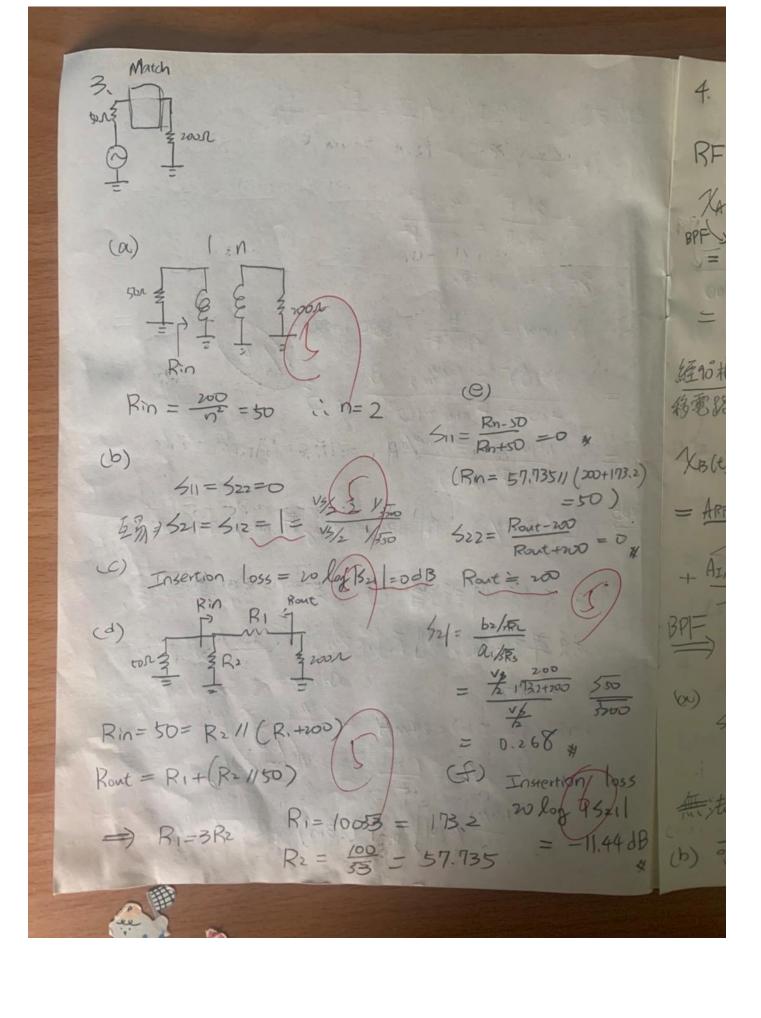

WIM-WED= WID WRF RF= ARFOS WAFT + AIM OB WIMT XACT) = (ARF LOS WRFT + ALM LOS WENT) ALO SIN WLO + BPF J ARFALO SM (WLO-WRF) + AIMALO SM (WD-WEM) + = ARFALO SIN (WLO-UPF) t. - ALMALO SIN (WEN-WLO) t 經验 -ARF ALO COS (WIO-WRF) + AIMALO COS (WIM-WO)t XB(t) = (ARF COS WRFT + AIM COS WIMT) ALO COS WLO t = ARFALO COS (WRF-WLO) + + AIMALO COS (WIM+WLO) + + AIMALO COS (WIM-WLO) + BPF ARFALO LOS (WRF-WIO) + ASMALO
2 COS (WIM-WIO) t Signal = XB(t) + X(t) (5 = AIMALO COS (WIM-(ULO)+ 無法得到想要的RF訊號 11.44 dB (b) 可将 % 相移電路由A鼓向B

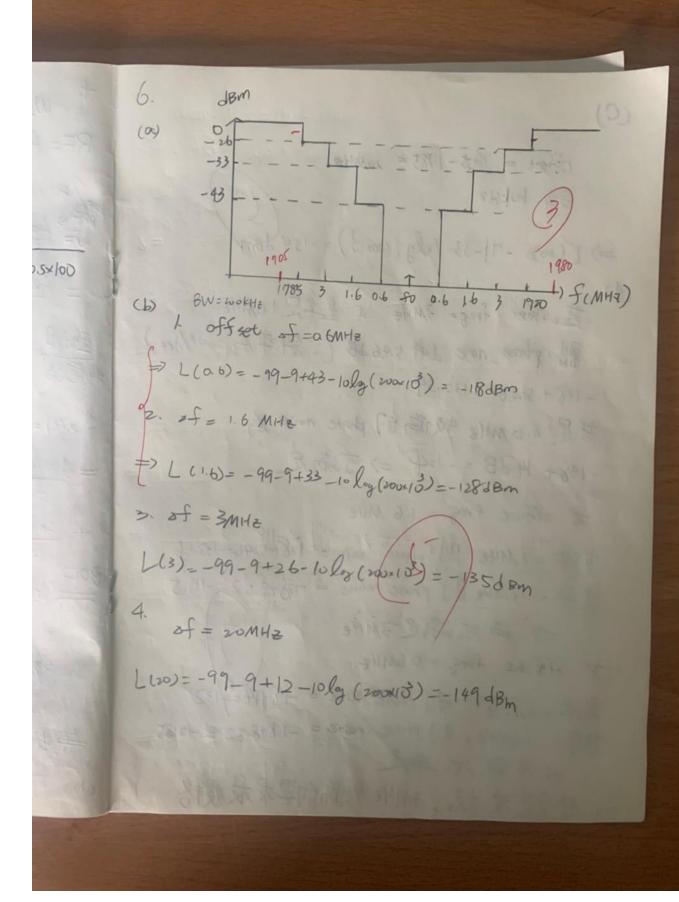(a) 先将dB轉為實際值再代公式 (00) NF= F, + F2-1 + F3-1 GIGZ + ... $= 2 + \frac{20-1}{10} + \frac{2-1}{10\times31.62} + \frac{10-1}{10\times31.62\times0.5\times100} + \frac{2-1}{10\times31.62\times0.5\times100}$ = 396= 5.976 dB (5) (b) Total gain 10+15-3+20-3=39 (dB) (1) (W -93+39=-54 dBm (5) (d) 1 OIP3 = OIP3, G2...Gn + OIP3, G3...Gn + ... $=\frac{1}{1910+281+0+50+0=0.0272}$ -15.654dBm L (20) = Ozp3 = 15.654 &Bm



(C) Offset = 1805-1785 = 20MHz BW= lookHZ => L(20)= -7 |-33-10ly (100+13) =-154 dBm (d) 苦 Offset freg= 3M4z f 基準是 1.6MHz Dy phase noise IA 5.46 dB (: 斜率為 200B/dec) -138+546=-13254 若是 0.6 MHs 频偏的 phase noise 為 -138+14dB=-124 => 可满足 # offset freg = 1-6 MHZ 其準=3M42 別 phase noise=-128-5.46-133.46 其準 = 0.6MUa Di) phase noise = -18+8.52=-19.5 为無法满足3MHz to offset freq = 0.6MHz 其準=3MHz , 凤J phase node = -118-14= +132 # = 1.6MHE A) phase noise = -118-8,52 = 1265 习皆無法满足 、整體束說,3MHR频偏的要求最嚴格